



# BIST implementation

---

## Group-4

Sasanka Uppuluri(2019102036)

Siva Durga(2019102038)

Viswanadh (2019112011)

Mani Teja(2019102023)



# Introduction



BIST – Built-in Self testing



We add additional circuits to the original function blocks to enable testing the circuit by itself



Has a wide variety of uses including cost reduction, testing time reduction.



Used to avoid the usage of ATE (Automated Test Equipment) which is considered rather costly.

## Advantages of BIST



Lower test costing



Testing is independent of future technology



Better fault coverage



Shorter test time



Easier customer support

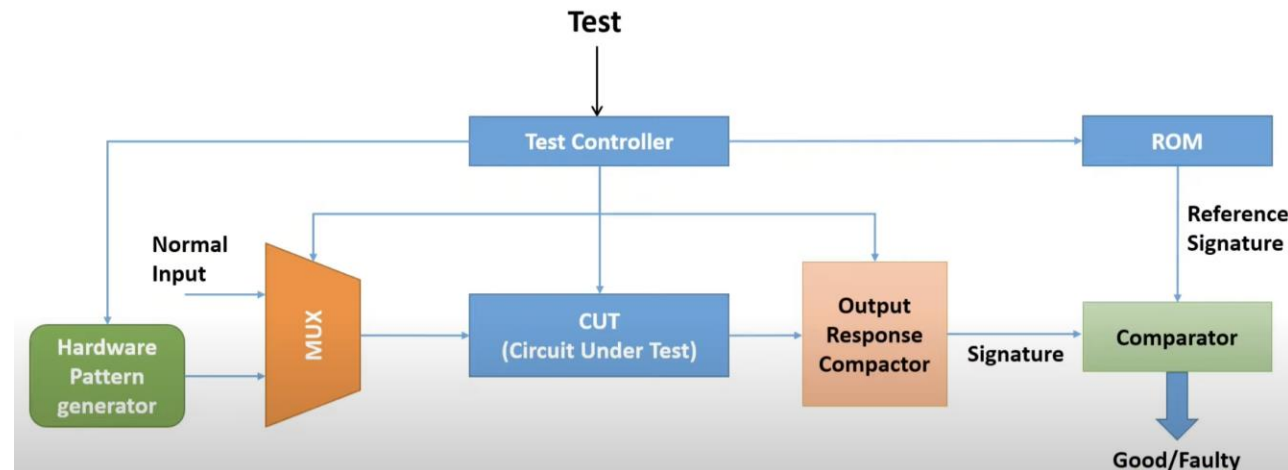


Fig: Basic architecture of BIST



# Implementation

- **Test Pattern Generator and Response analyzer**
  - Test Pattern Generator and Response Analyzer are often implemented using Linear-Feedback Shift Registers (LFSR).
  - The LFSR is an n-bit shift register which pseudo-randomly scrolls between  $2^n - 1$  values.
  - The Pseudo-Random Pattern Generator generates the necessary patterns which are fed as inputs to the CUT.
- **Circuit Under Test(CUT)** [Figure on the top-right]
- **Comparator**
  - A simple n-bit comparator has been used to compare the fault-free signature with the faulty one.

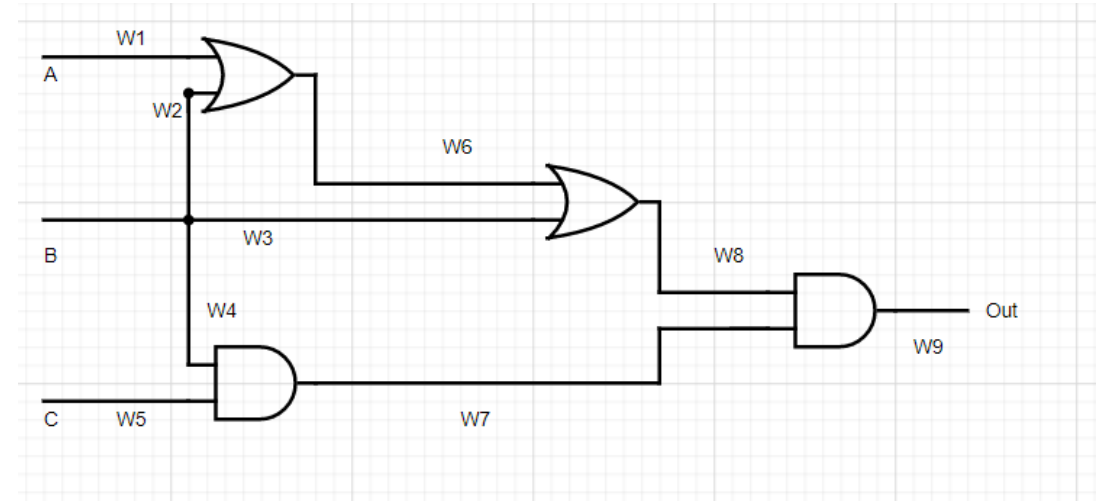


Fig: Circuit Under Test


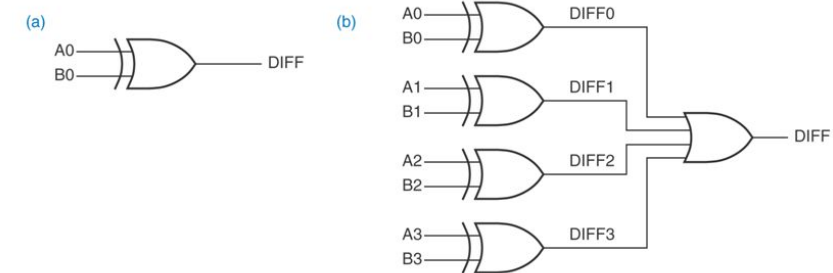


Fig: Comparator
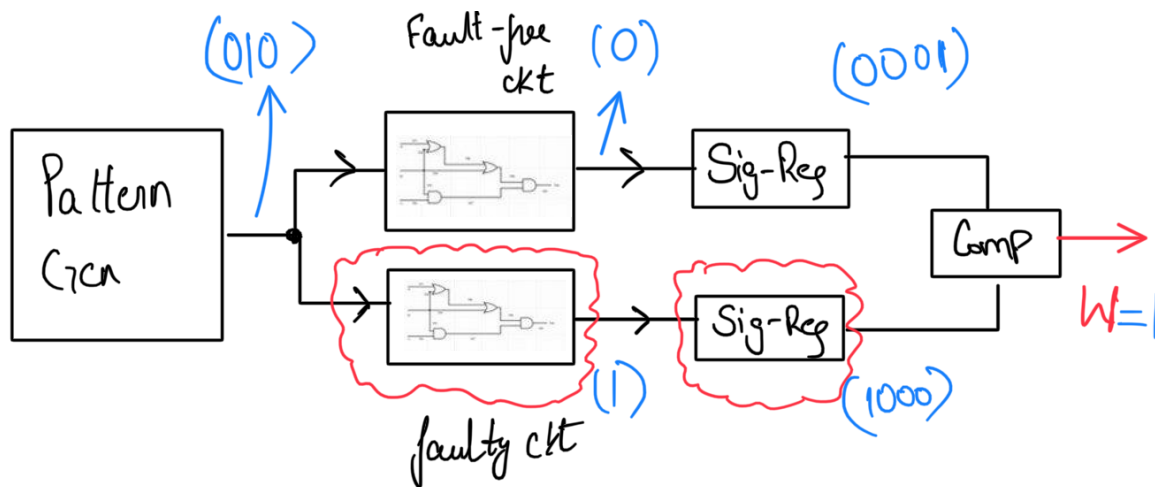
## Working and Results


- If there's a s-a-f in faulty circuit (here w7 is stuck at 1) then output's get toggled, setting the comparator output to 1 which indicates that the CUT is faulty



Error	Comp Output (W)
Not Present	0
Present	1
 
# Work Done

- Implemented an ideal Online-non concurrent BIST.
- Consists of five main modules: Implemented each in verilog
- Implement a flexible combinational circuit where stuck-at-faults can be given as arguments to the module instead of hardcoding.
- Prepared a wrapper ALU to integrate all the individual modules and designed a testbench for the same
- Testbench includes 3 different cases: I) ckt with 0 saf, ii) fault-free ckt, iii) ckt with 1 saf



Truth table

A	B	C	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

stuck at faults

$w_i = \text{check}[i]$

Val = stuck at fault  
location value

